

CONTENT

1. EXPERIMENT 1

Presentation of the laboratory platform

1. The purpose of the laboratory assignment	9
2. Theoretical aspects	9
2.1. Description of the laboratory platform.....	9
2.1.1. Description of the multifunctional platform	9
2.1.1.1. Description of the power supply unit.....	11
2.1.1.2. Description of the block of automatic clock generators	11
2.1.1.3. Description of the automatic clock formers block.....	13
2.1.1.4. Description of the block of manual beat generators.....	14
2.1.1.5. Description of the block of frequency dividers	15
2.1.1.6. Description of the block of free pins	16
2.1.1.7. Description of the key block.....	17
2.1.1.8. Description of the parallel data entry block.....	17
2.1.1.9. Description of the signaling block.....	18
2.1.1.10. Description of the 7-segment display block	18
2.1.2. Description of the mounting platform.....	19
3. Procedure of work progress	19
3.1. Power block testing.....	19
3.2. Testing the block of automatic clock generators	20
3.3. Testing the automatic clock formers block	20
3.4. Manual clock former block testing	21
3.5. Frequency divider block testing.....	21
3.6. Testing the block with free pins	22
3.7. Testing the key pad block	22
3.8. Testing the parallel input block.....	22
3.9. Testing the signaling block	22
3.10. Testing the 7-segment display block.....	22
3.11. Procedure	23

2. EXPERIMENT 2

The analysis and synthesis of combinational logic circuits

1. Theoretical aspects	24
2. Procedure of work progress	28
3. The content of the report	28

3. EXPERIMENT 3

The even/odd parity detector

1. Theoretical aspects	29
2. Procedure of work progress	35
3. The content of the report	36

4. EXPERIMENT 4

Code Converter

1. Theoretical aspects	37
2. Procedure of work progress	42
2.1. "Natural Binary Code" - "Gray" cod converter study	42
2.2. "Gray - natural binary" code converter study	43
3. The content of the report	43

5. EXPERIMENT 5

Digital comparators

1. Theoretical aspects	44
2. Procedure of work progress	50
2.1. Implementation of 1-bit comparator	50
2.2. Study of the 4-bit comparator	50
2.3. Study of the 8-bit comparator	50
3. The content of the report	51

6. EXPERIMENT 6

Adders

1. Theoretical aspects	52
2. Procedure of work progress	58
2.1. Study of the half-adder	58
2.2. Study of 1-bit full adder	58
2.3. Study of the 4-bit full adder	58
3. The content of the report	59

7. EXPERIMENT 7

Study of a data transmission system

Part I: The multiplexer

1. Theoretical aspects	60
2. Procedure of work progress	65
3. The content of the report	65

Study of a data transmission system

Part II: The demultiplexer

1. Theoretical aspects	66
2. Procedure of work progress	70
3. The content of the report	71

8. EXPERIMENT 8

Address decoders and coders

1. Theoretical aspects	72
2. Procedure of work progress	81
2.1. Study of the address decoder	81
2.2. Study of the address coder	82
2.3. Study of the address coder-decoder assembly	82
3. The content of the report	82

9. EXPERIMENT 9

BCD-Decimal decoders and BCD-7 Segments

1. Theoretical aspects	83
2. Procedure of work progress	87
3. The content of the report	87

10. EXPERIMENT 10

Latches and Flip-Flop

1. Theoretical aspects	88
1.1. RS Latches	88
1.1.1. Asynchronous RS Latches	88
1.1.2. Synchronous RS flip-flop.....	91
1.1.3. “Master-Slave” RS flip-flop.....	93
1.1.4. D latch	94
1.1.5. JK flip-flop.....	95
1.1.5.1. Synchronous CBB-JK.....	95
1.1.5.2. JK flip-flop Master Slave	96
2. Procedure of work progress	96
2.1. Study of the asynchronous RS-Latches, NOR/NAND variant	96
2.2. Study of the synchronous RS flip-flop, NAND&NOR variant.....	96
2.3. Study of the “Master-Slave” RS flip-flop	96
2.4. Study of the “Master-Slave” JK flip-flop	97
2.5. Study of the synchronous D <i>flip-flop</i> ,	97
3. The content of the report	97

11. EXPERIMENT 11

Registers

1. Theoretical aspects	98
2. Procedure of work progress	107
2.1. The study of the parallel register regime	107
2.2. The study of the series shift register	108
2.3. The study of the parallel-serial register (converter).....	108
2.4. The study of the series-parallel register (converter)	108
3. The content of the report	108
Annex	109
Bibliography.....	113